 


**Choose the right A/D converter  
for your application**

# Agenda

- Analog-to-Digital-Converters (ADCs)
  - What are the Signal Frequencies
    - Analog Classes of applications
    - Frequency ranges of ADCs
  - Nuts and Bolts of Delta-Sigma Converters
  - The SAR ADC
  - The High-speed Pipeline Topology
- Digital-to-Analog-Converters (DACs)
  - R-2R-DACs
  - String-DACs
  - Multiplying DACs
  - Delta-Sigma DACs
  - High-Speed Current-Steering DACs


# Real World vs. Bandwidth




# ADC Architectures

- **There are many different ADC Architectures**
  - **Successive Approximation (SAR)**
  - **Delta-Sigma ( $\Delta\Sigma$ )**
  - **Pipeline**
  - **(Flash)**
- **Delta-Sigma converters determine the digital word by**
  - **Oversampling**
  - **Applying Digital Filtering**
- **SARs determine the digital word by**
  - **Sampling the input signal**
  - **Using an iterative process**
- **Pipeline converters determine digital word by**
  - **Undersampling**
  - **With Sample / Gain Algorithm Topology**
  - **Multiple stages / Larger Cycle-latency**


# ADC Technologies - $\Delta\Sigma$

 

# ADC Technologies - SAR

 

# ADC Technologies - pipeline

 

# Selecting ADC Topology

<b><i>ADC Topology</i></b>	<b><i>F Conversion</i></b>	<b><i>Resolution</i></b>	<b><i>Comments</i></b>
<b>SAR</b>	$\leq 4\text{Msps}$ $\leq 1.25\text{Msps}$	$\leq 16\text{-bit}$ $\leq 18\text{-bit}$	<b>Simple operation, low cost, low power.</b>
<b>Delta-Sigma</b>	$\leq 4\text{ksps}$ $\leq 4\text{Msps}$ $\leq 10\text{Msps}$	$\leq 31\text{-bit}$ $\leq 24\text{-bit}$ $\leq 16\text{-bit}$	<b>Moderate cost.</b>
<b>Pipeline</b>	$\leq 200\text{Msps}$ $\leq 250\text{Msps}$ $\leq 550\text{Msps}$	$\leq 16\text{-bit}$ $\leq 14\text{-bit}$ $\leq 12\text{-bit}$	<b>Fast, expensive, higher power requirements.</b>




# Which ADC Architecture to Use??

Characteristic	Pipelined	SAR	Delta Sigma
Throughput (samples/sec)	++	+	0/+
Resolution (ENOB)	0	+	++
Latency (Sample-to-Output)	+	++	0
Suitability for converting Multiple Signals per ADC	+	++	0
Capability to convert non-periodic multiplexed signals	+	++	-
Power Consumption	Scales with Sample Rate or Constant	Scales with Sample Rate	Constant

# Applications for $\Delta\Sigma$ Converters


- Signal Level – System clock range ~ 0.5 to 40 MHz
  - Has an Internal Digital Low-Pass Filter
    - Uses an integrator
  - Accurate near DC
  - High Resolution – up to 24 bits
- Audio – System clock range ~ 20 to 40 MHz
  - Has an Internal Digital Low-Pass Filter
  - Optimized noise performance
  - Optimized filter in audio frequency for flatness

# Delta-Sigma A/D Converters

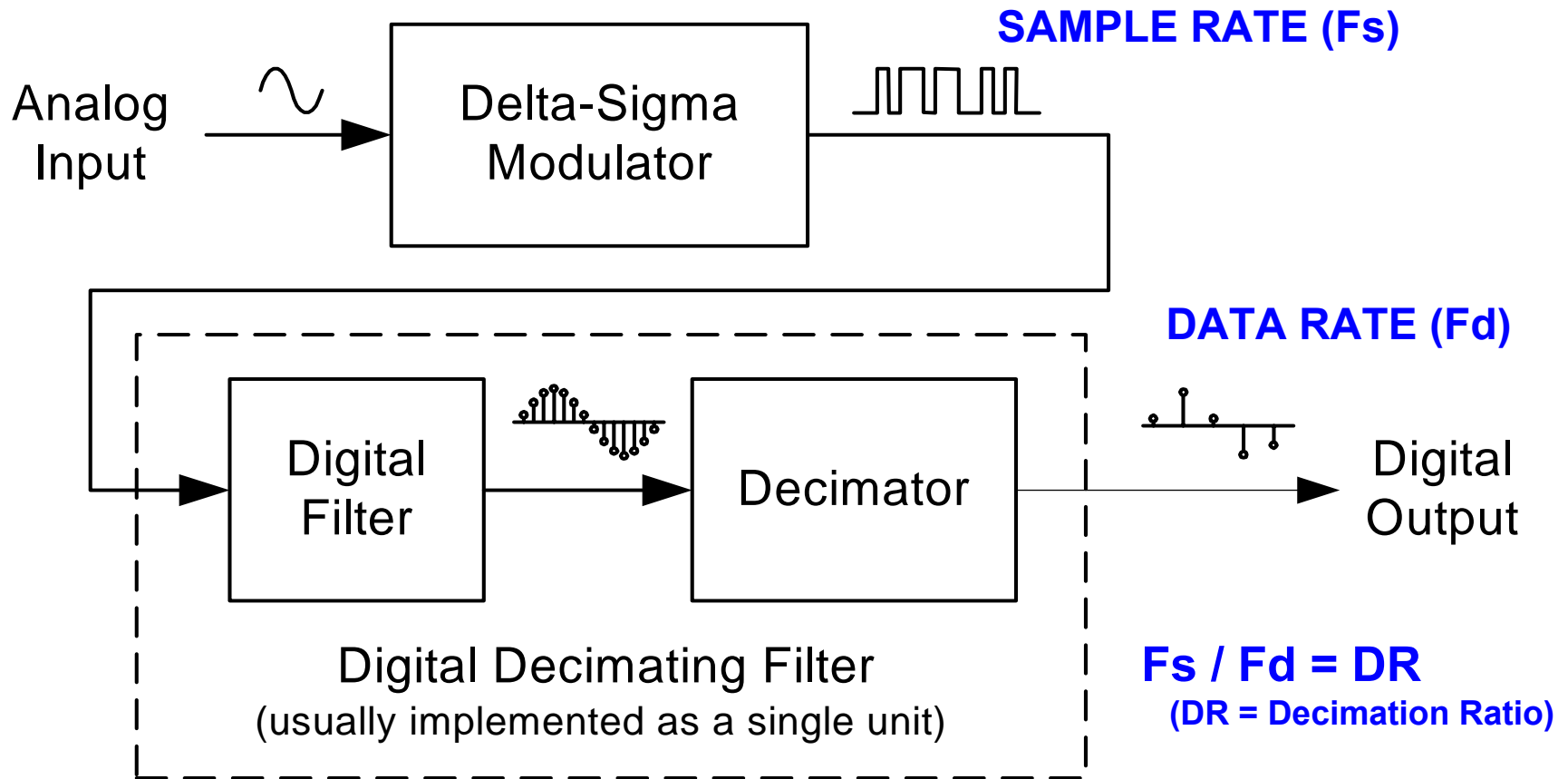


# Input to the Delta-Sigma A/D

*You are here*

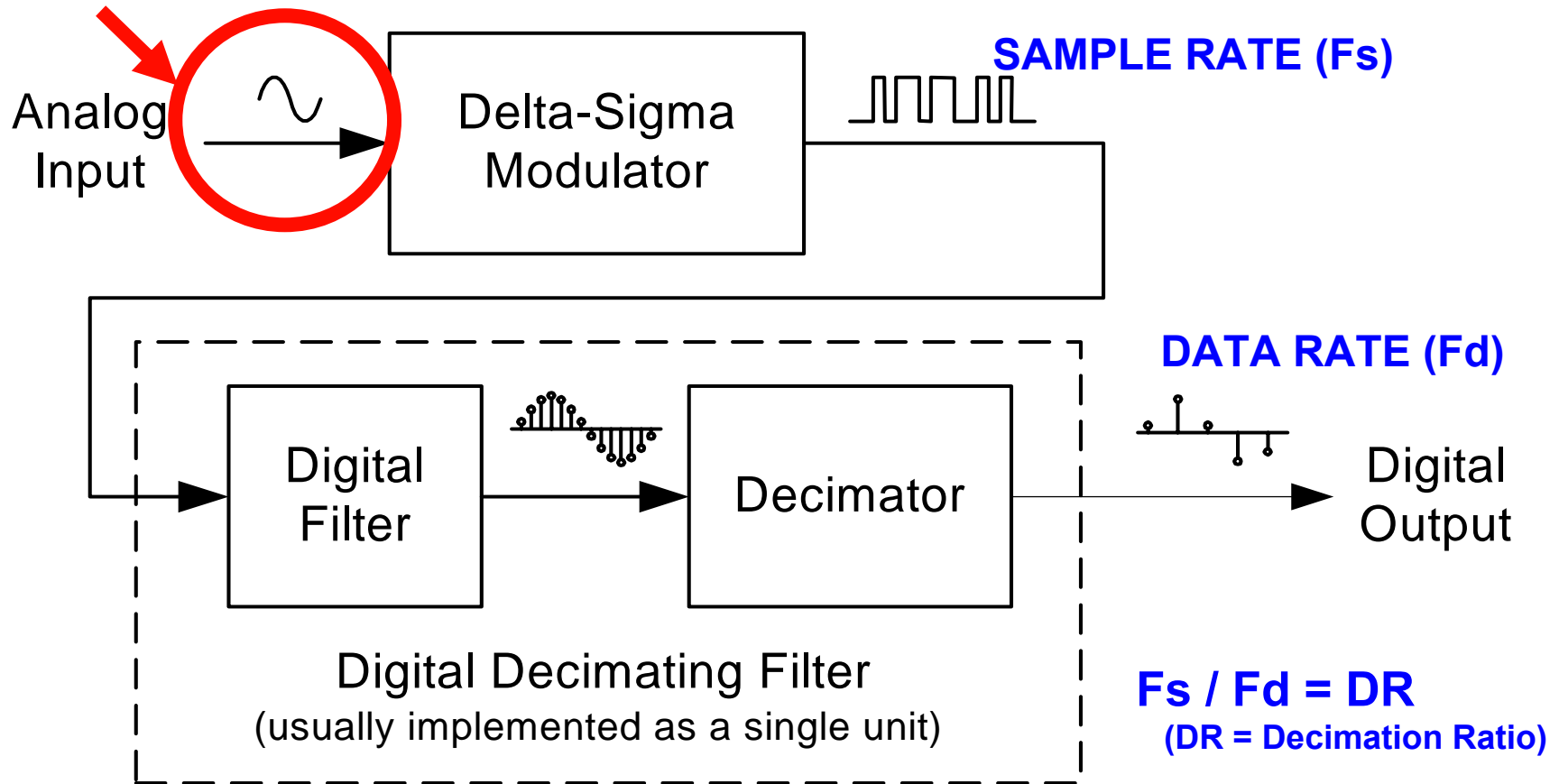


# Input Signal


**Input Signal:  
TIME DOMAIN**

 

**Input Signal:  
FREQUENCY DOMAIN**

 


# Modulator Output

 


# 1<sup>st</sup> Order Delta-Sigma Modulator

## TIME DOMAIN

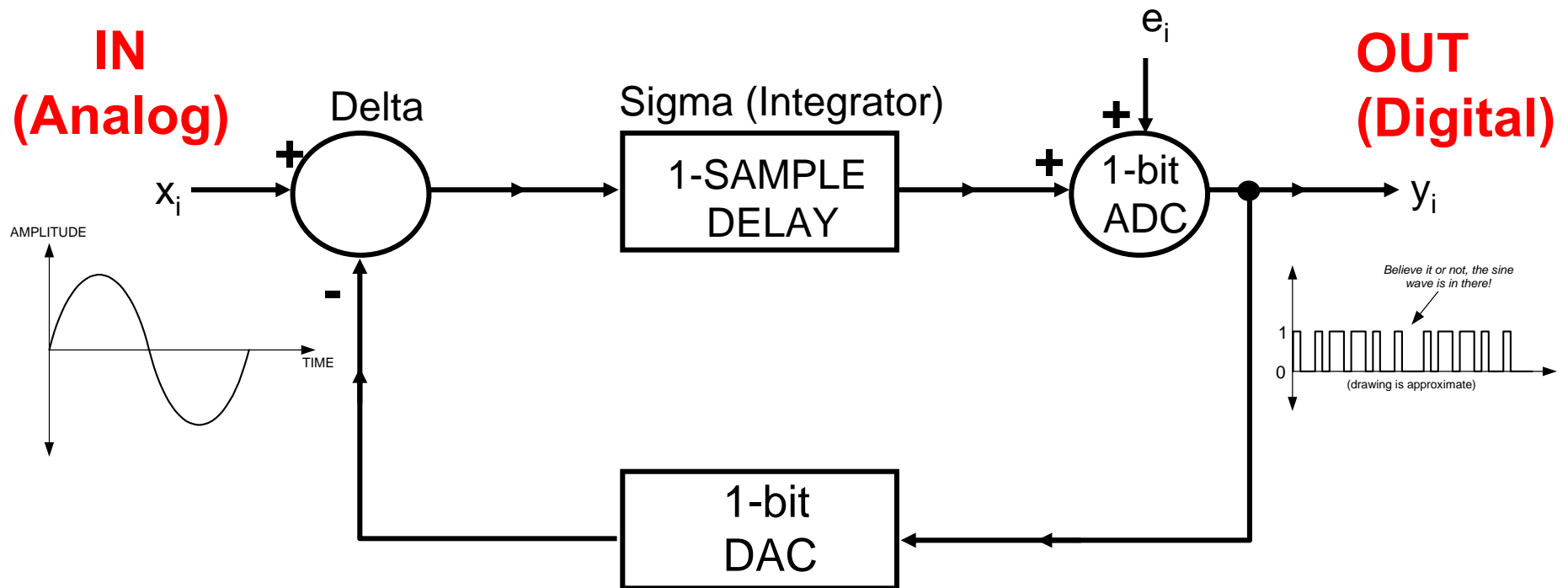


# Modulator Output Signal

**Modulator Output:  
TIME DOMAIN**

 


**Modulator Output:  
FREQUENCY DOMAIN**

 





# Multi-order Delta-Sigma Modulators

 


# Delta-Sigma A/D Signal Path

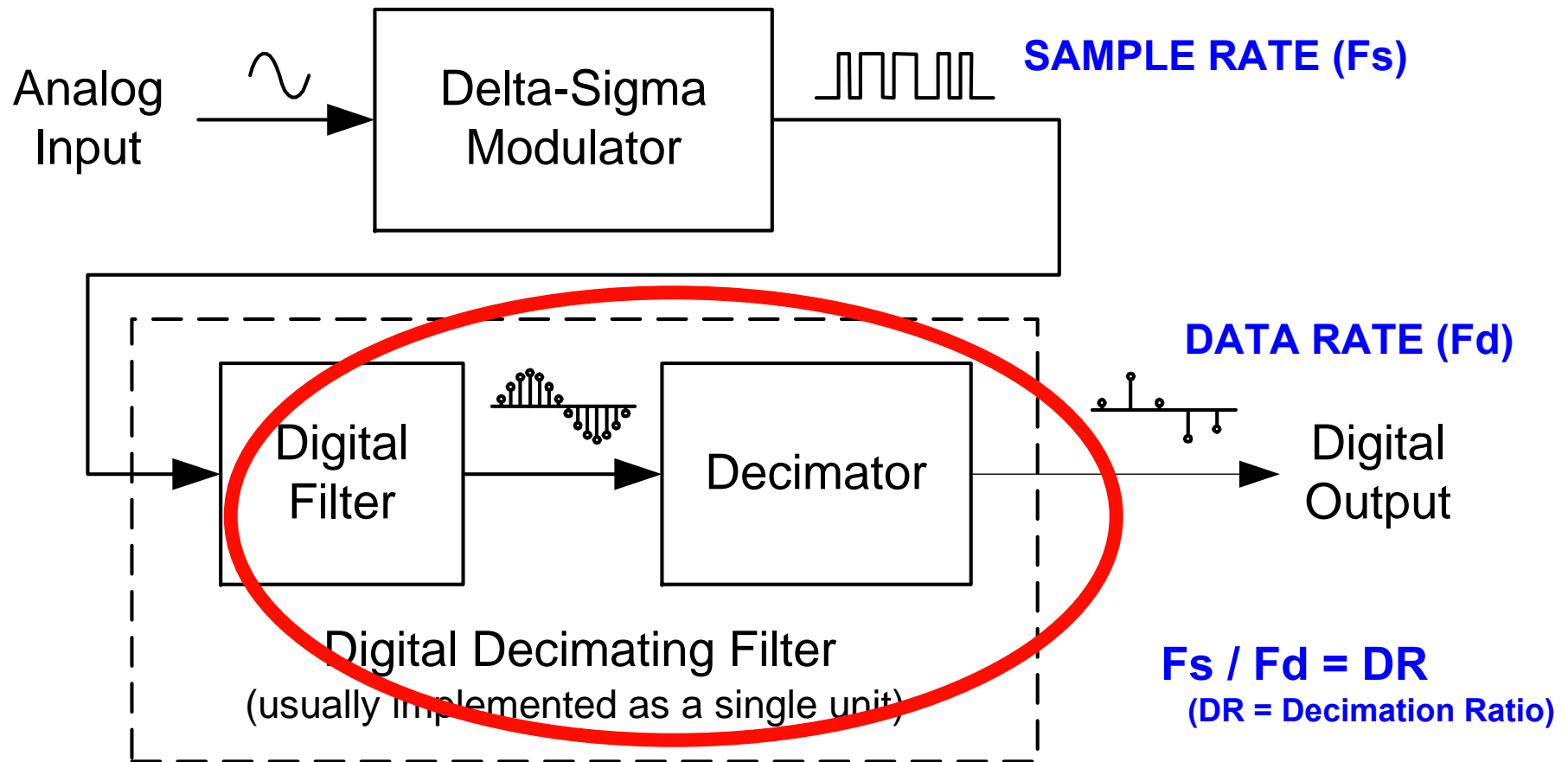


# Digital Filter Function

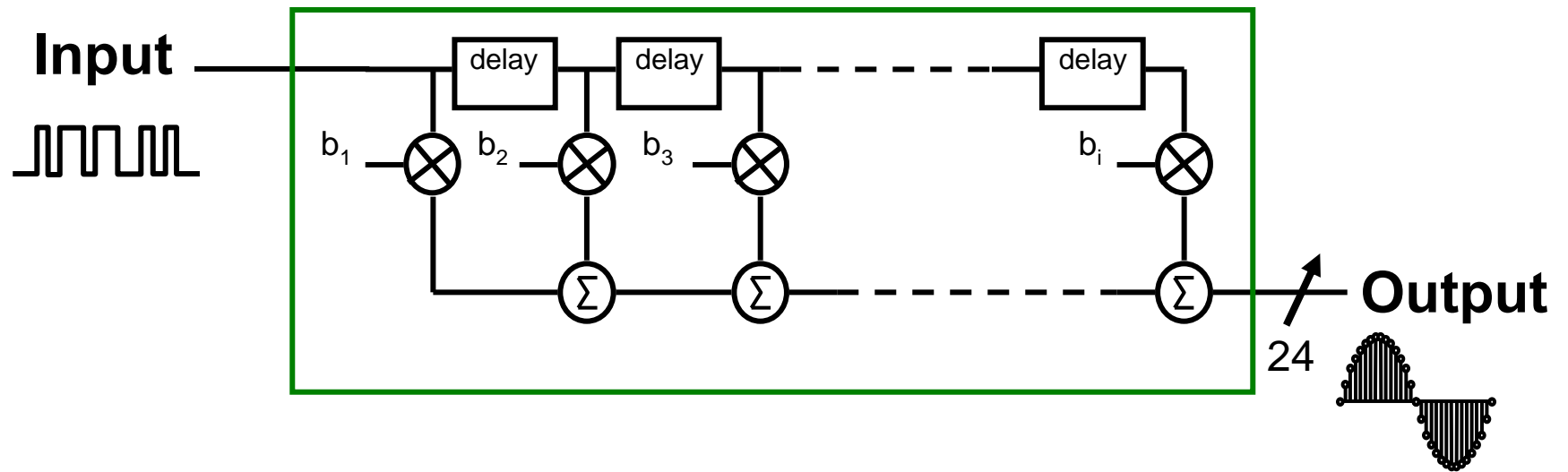

# High Frequency Noise Reduction

 


# Sinc3 Filter response

 


# Outcome of Digital Filter Function


TIME DOMAIN

 

# Decimation Digital Filter

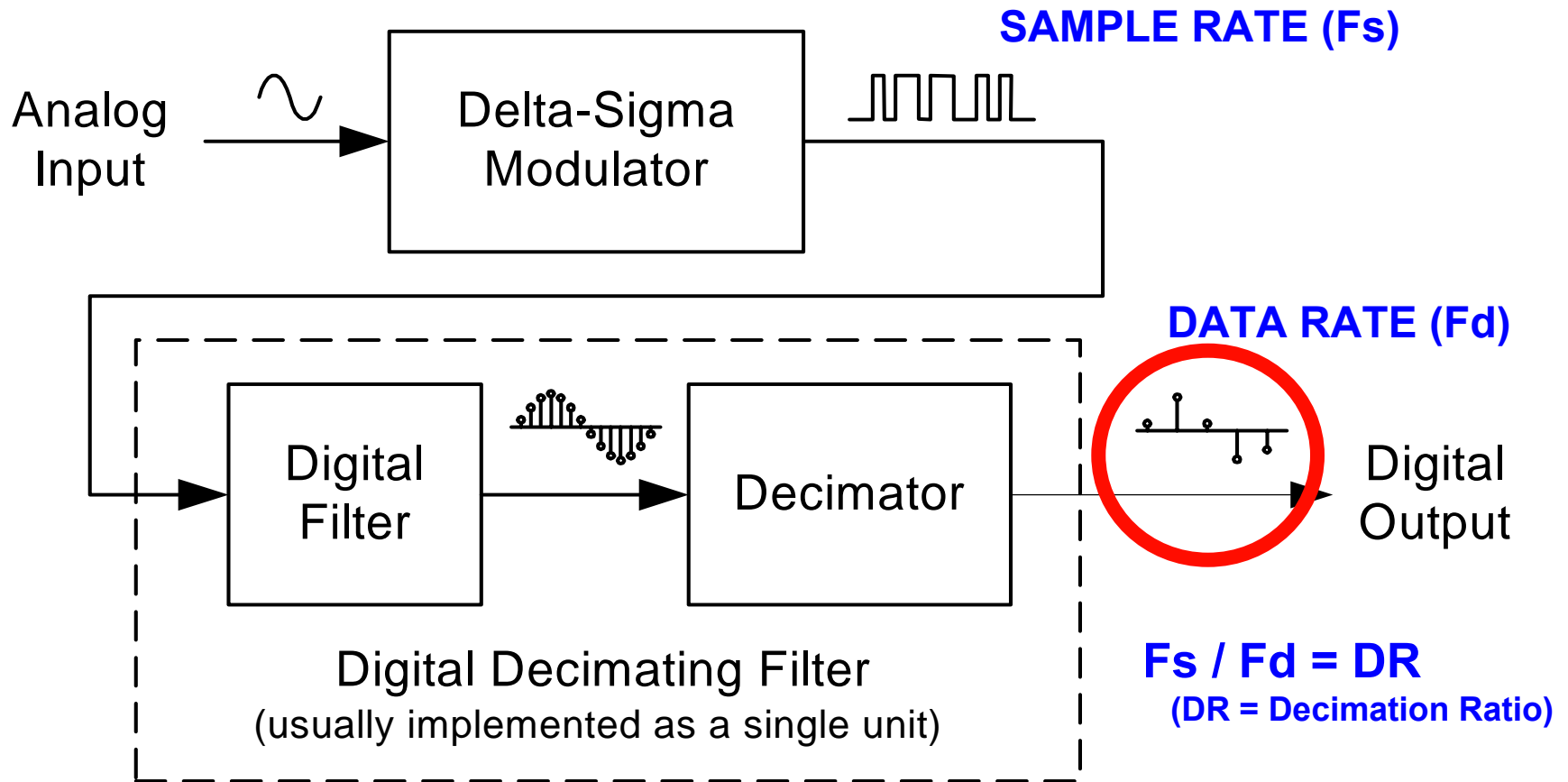


# Decimator Function: Averager

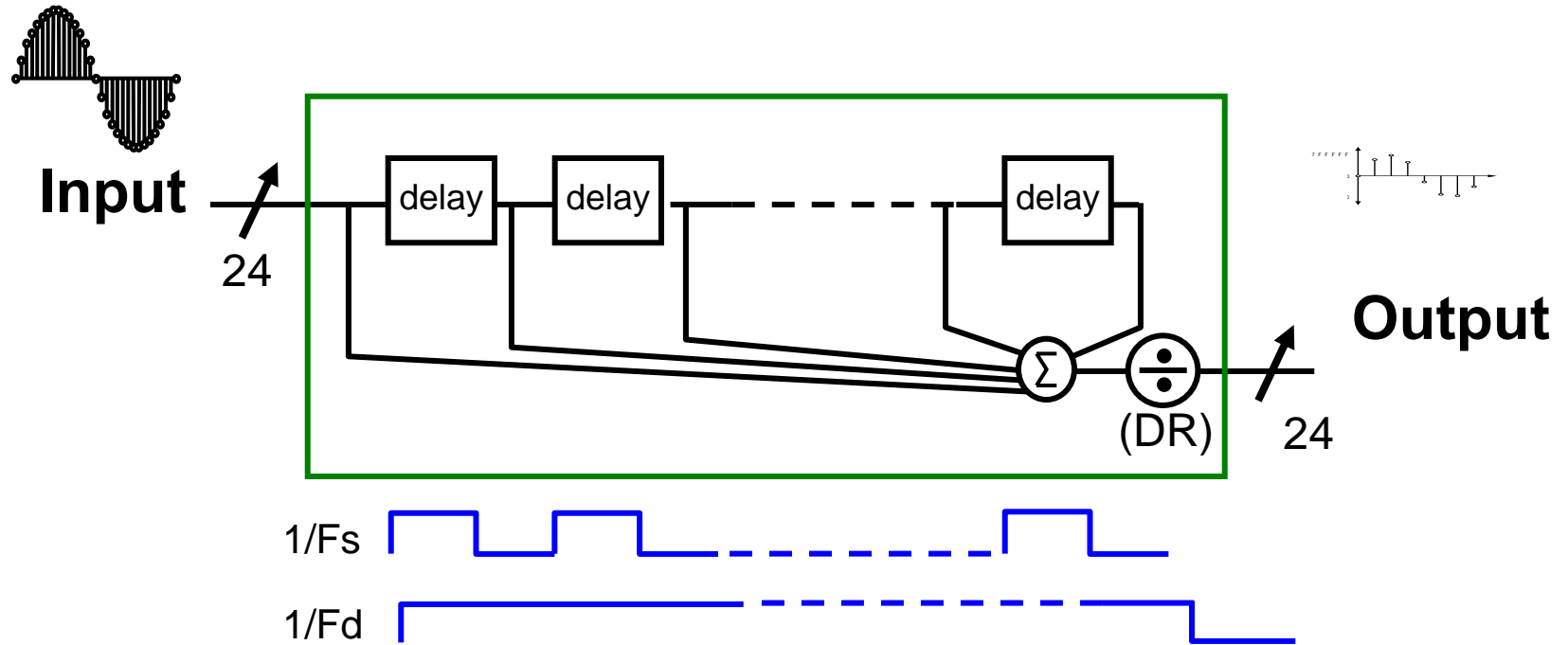




# Decimator Function: Pick & Dump

 


# Sampling speed vs. SNR

$$F_s / F_d = DR = K$$

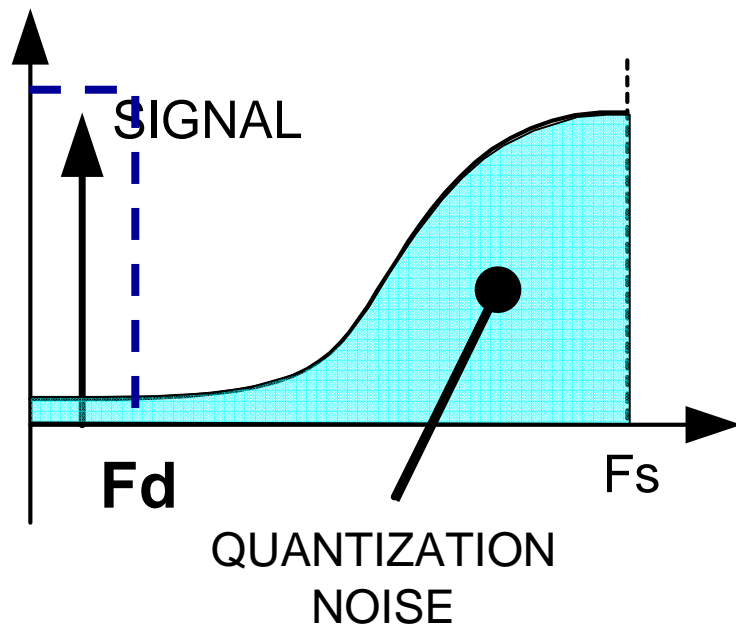

A.

$$DR_A > DR_B$$

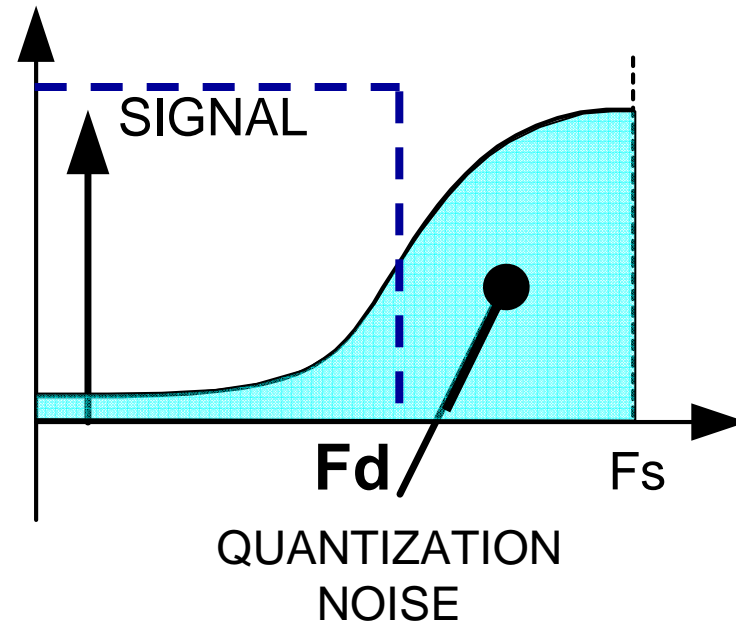

B.


# Additional Features

$\Delta\Sigma$ s often have additional features for data acquisition

- Analog PGA (ADS1282, ADS1248/7/6, ADS1230/2)
- Input Buffer (ADS1222/4/5/6, ADS1245, ADS1259)
- Burnout Current Sources (ADS1243/44)
- Multiplexers (most ADS12xx)
- More complete system solution (ADS1248, ADS1115)
- Sensor Excitation (ADS1248/7)
 
# The SAR ADC


- Most Serial ADCs are SARs or Delta-Sigmas
- SARs are Best for General Purpose Apps
  - Data Loggers,
  - Temp Sensors,
  - Bridge Sensors,
  - General Purpose
- In the Market SARs
  - Can be 8 to 18 bits of resolution
  - Speed range: > DC to < 5 Msps
- SARs found as
  - Stand-alone
  - Peripheral in Microcontrollers, Processors




# How Does a SAR work?

- Similar to a balance scale

the MSB is determined first

 


# SAR Conversion Concept

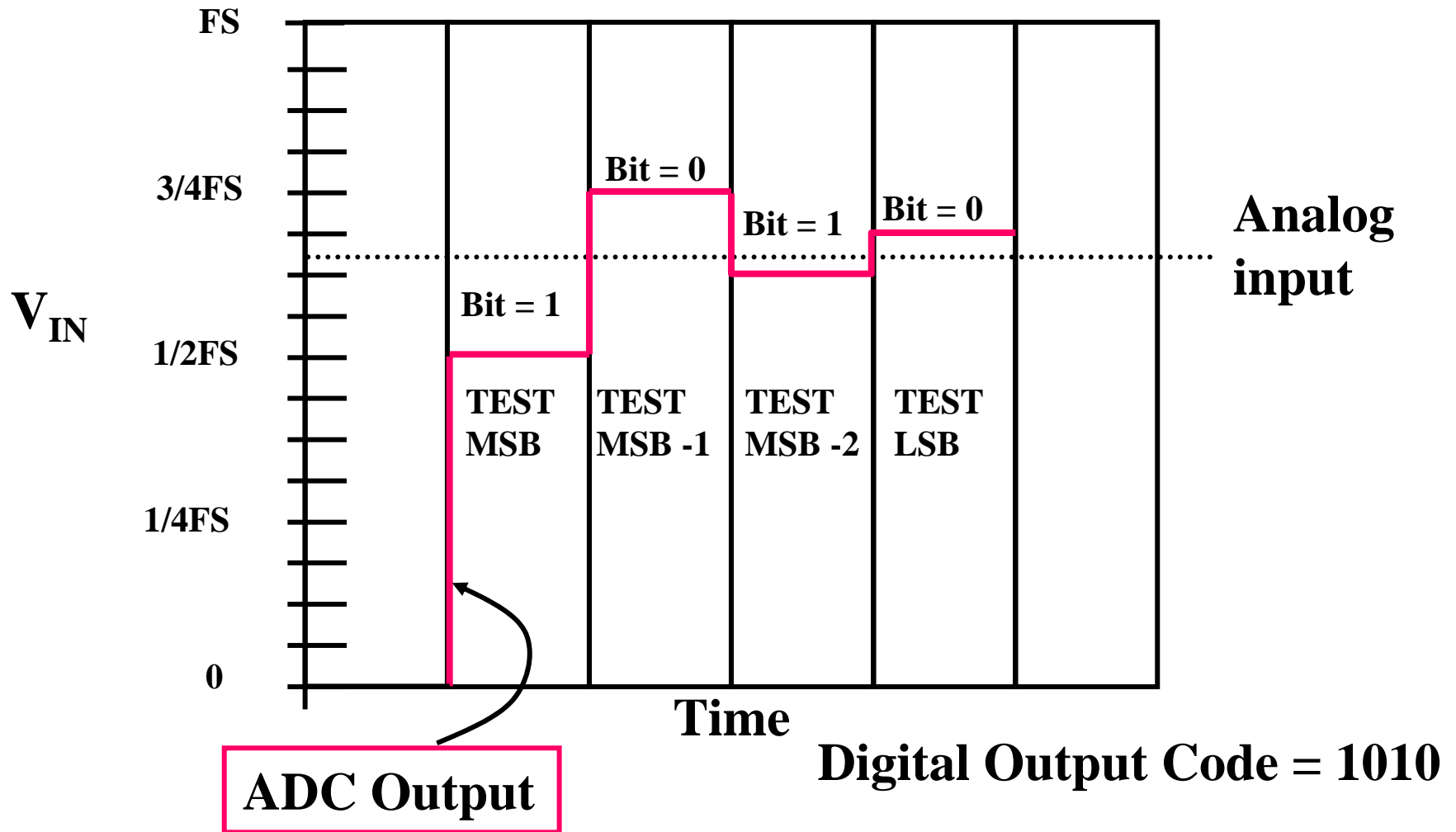

# SAR Converter – Input Stage

## SAR ADC

 

Note: All capacitors must be able to charge to  $\frac{1}{2}$  LSB within the acquisition time!

# Additional Features


- Fewer options with SARs
  - Some converters have multiplexers (ADS82xx)
  - References (ADS78xx, ADS84xx, ADS85xx, etc.)
  - Input Buffers/Drivers (ADS8254/55/84)
  - PGA (ADS7870/71)
  - Programmable Alarm Level Comparator (ADS795x)




# High Speed – Pipeline Topology

- Pipeline converters fit high-speed applications (5 MHz to >100MHz).
- Applications where you typically find pipeline converters are:
  - Wireless and Line Communications
  - Test and Measurement, Instrumentation
  - Medical Imaging
  - Radar Systems
  - Data Acquisition
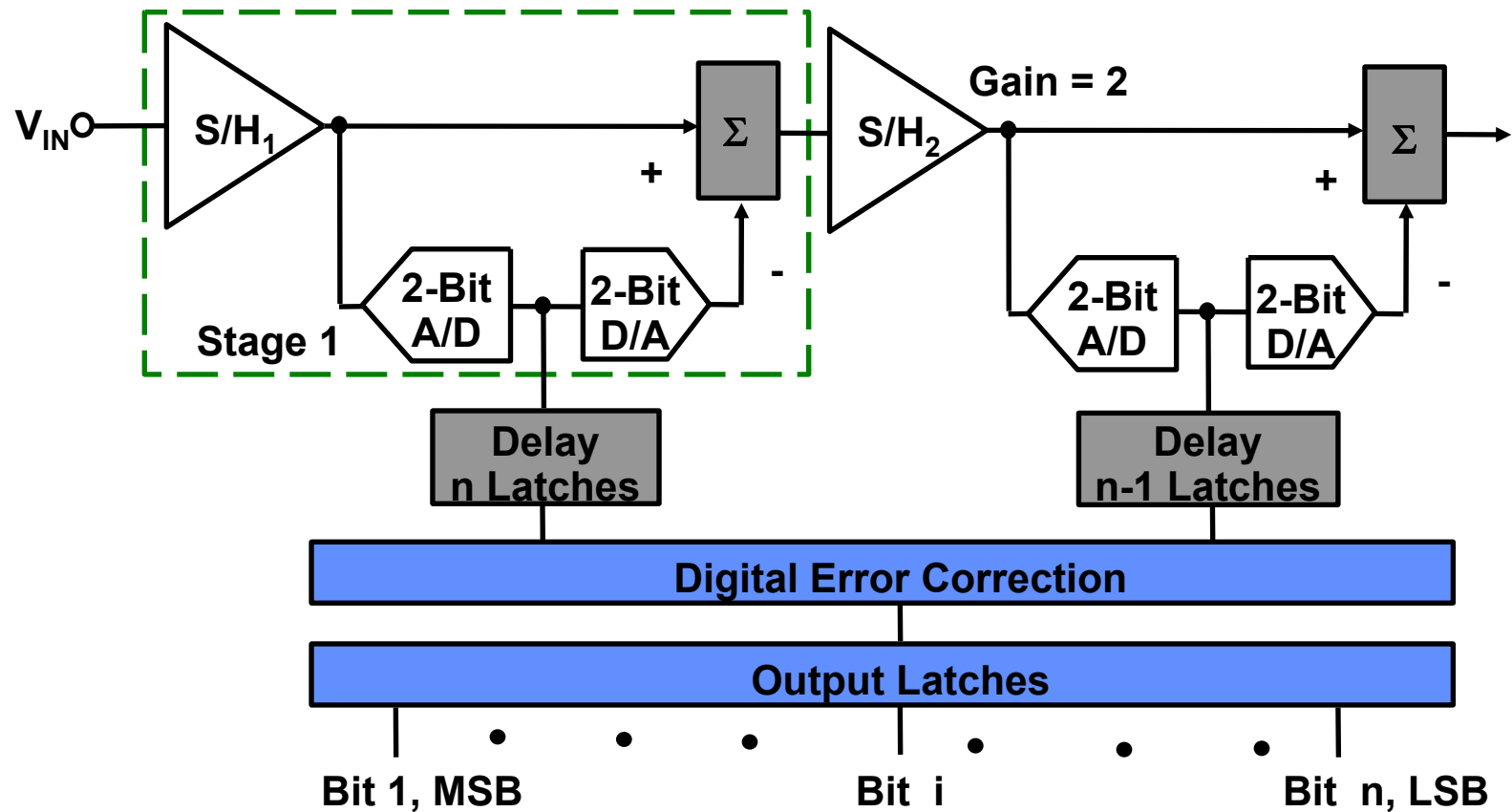
# Pipeline A/D Converter Architecture Overview



# System

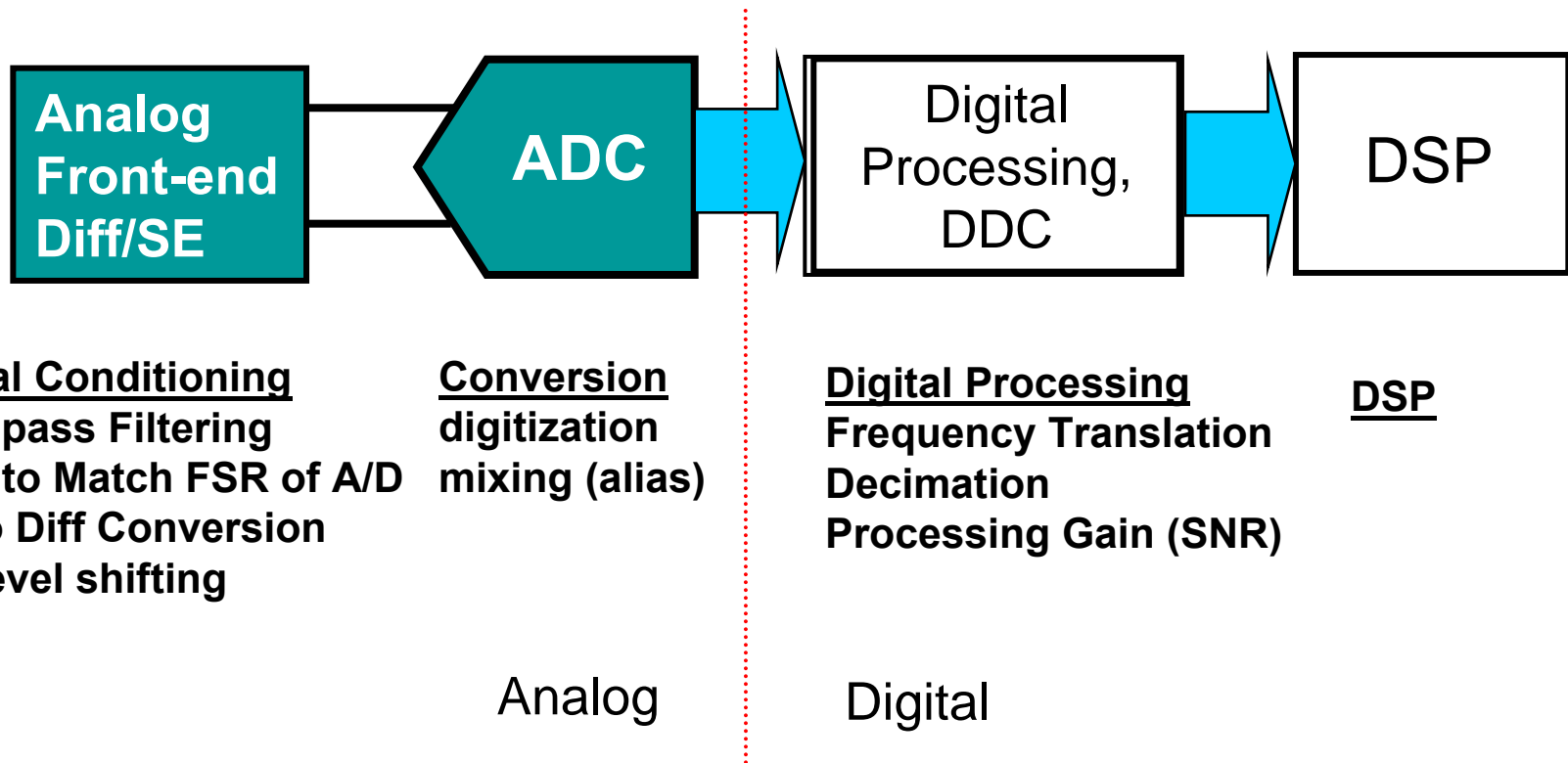

# What's the Application?

## Time Domain

- **Imaging (CCD)**
  - Camcorders
  - Digital Cameras
  - Scanner
  - RGB/Comp. Video
  - Test Instrumentation
  - Medical
- **Important Specs:**
  - SNR
  - Slew-Rate/ tset
  - DNL
  - DC-Accuracy/ Drift


## Frequency Domain

- **Communications**
  - Set-Top Box
  - Cable Modem
  - Basestation
  - IF Digitizer
  - GPS
  - Frequency Synthesizer
- **Important Specs:**
  - SFDR
  - ENOB
  - Analog Input Bandwidth
  - Jitter

# ADC Interface Solutions


## Principle Configuration Choices

### Single-Ended Input (SE)

 

Requires full input swing from  $+fs$  to  $-fs$   
 2x the swing compared to differential  
 Input signal at IN typically requires a  
 common-mode voltage for bias  
 Input  $\overline{IN}$  also requires a  $V_{cm}$  for correct  
 dc-bias

### Differential Input (DE)

 


Combined Differential inputs result in  
 full-scale input of  $+fs$  to  $-fs$   
 Each input only requires 0.5x the  
 swing compared to single-ended  
 Both inputs require a  $V_{cm}$  for correct  
 dc-bias

# SE vs. DE Issues


- Single-ended Inputs (SE)
  - Degraded dynamic performance (larger FSR)
  - Common-mode voltage and op amp headroom may limit use for dc-coupling
  - Best suited for Time Domain applications
- Differential
  - Optimized performance due to lower FSR, Reduction of even-order and common-mode components
  - Best for higher input frequencies (IFs)
  - More complex driver circuitry (consider Diff – Amps)
  - Best suited for Frequency Domain applications

# Driving Capacitive Input ADCs

 

- Due to Opamp's finite ( $R_O$ ) output impedance,  $V_{OUT}$  will drop momentarily when cap load is switched.
- As the output recovers, ringing may occur, which results in increased settling time.
- Use external  $R$ : isolates OpAmp output from capacitive load and improves settling.

# Differential ADC Driver

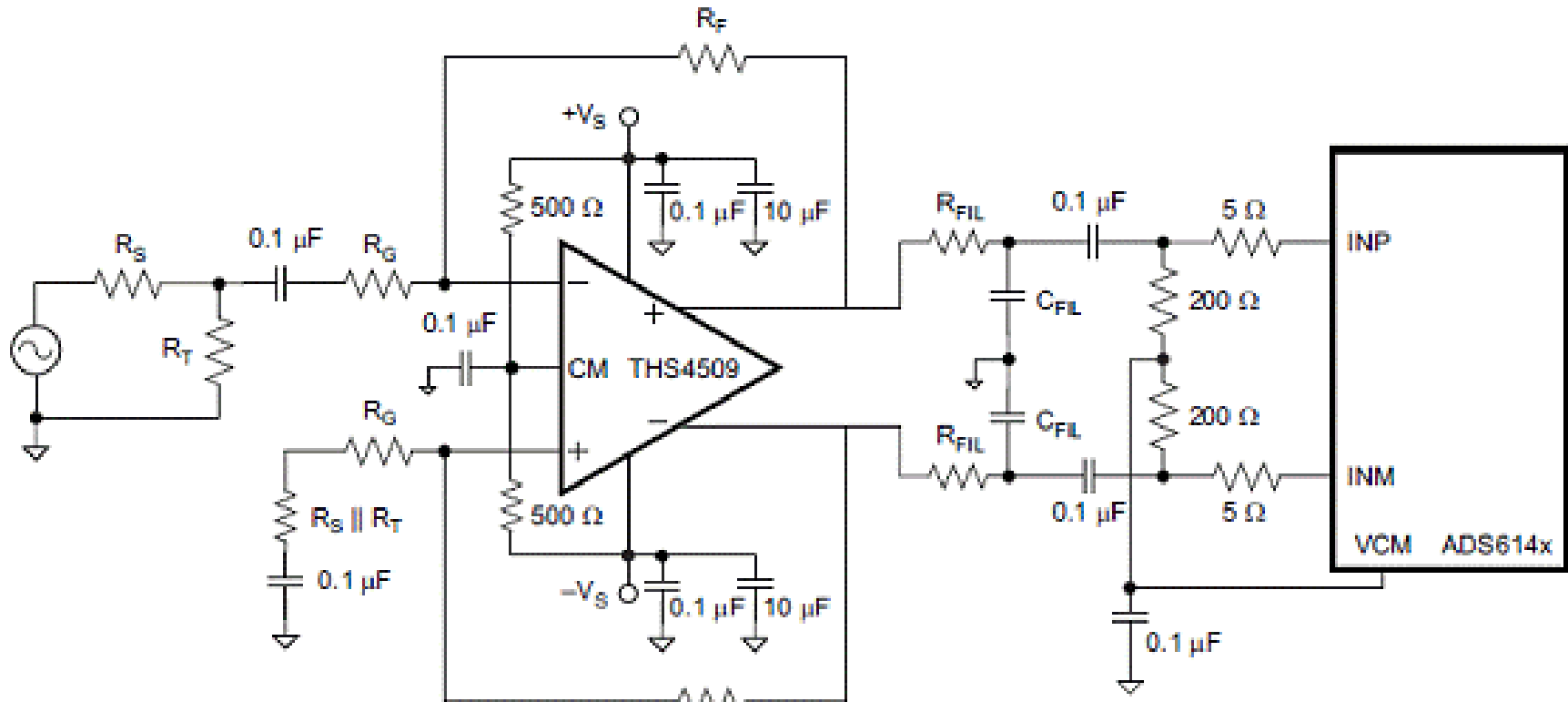

## Driver Solution:

- No Transformer
- VCM matched to ADC
- Good even-order harmonic rejection
- Easily configured for gain and low-pass filter



**Choose the right A/D converter  
for your application**

# What do you know about your signal?


- Desired Bandwidth?
  - up to 4MSPS SAR,
  - up to 10MSPS Delta Sigma,
  - above Pipeline
- Is DC precision important?
  - YES -> look at Delta Sigmas at first choice
  - alternative SAR Converters with DC Precision
- Does your signal have frequency content above Nyquist?
  - YES and it needs to be detected -> SAR or Pipeline with external Bandpass Filter
  - YES but can be ignored -> SAR or Pipeline, or Delta Sigma with Sinc Filter and an external Anti Aliasing Filter (AAF)
  - YES, but no external filter possible -> Delta Sigma with FIR
  - NO -> Delta Sigma with Sinc or FIR filter or SAR or Pipeline

# What do you need to find out about your signal?

- A specific point in time needs to be frozen?
  - YES -> Sample and hold Stage is needed like in SAR, Pipeline (no Delta Sigma)
- Can an average of your signal be used as long as the constant phase relation does exist?
  - YES -> Delta Sigmas can be used as they average the signal
- Do you need to convert multiple signals in phase relation to each other?
  - YES -> multiple synchronous S/H are needed or synchronous Delta Sigma Modulators – Multi Channel converters exist for all three types SAR, Delta Sigma, Pipeline
  - NO -> Multiplexing can be used. Exists for SAR and Delta Sigma.
 
# Desired resolution?


- SAR is available up to 18bit
- Delta Sigma is available up to 24bit
- Pipeline is available up to 16bit



 
# Is a latency tolerable?

Is the measured signal information needed immediately or can a delay be tolerated as long as it is constant?

- Immediate -> SAR or pipeline & high speed serial or parallel interface  
-> 0-cycle latency,  
1 Fdata delay



 - Delay -> Delta Sigma with 2-5 Fdata delay using SINC filter with serial interface SPI/I2C



- Huge delay -> Delta Sigma with multiple Fdata Delay from FIR with linear Phase (number of TAPS/2), e.g. 78 Fdata delay

# Strengths and definition of Linearity

- SARs have good monotonicity  
spec: INL / DNL
- Delta Sigma is monotonous by principle  
spec: THD
- Pipeline: due to the staged architecture (ADC-DAC-ADC...) non-linearities add-up  
spec: SFDR

# Input voltage range?

- Does it fit directly to an available ADC?
  - single ended or differential inputs exist
  - SAR ADCs offer unipolar or bipolar
  - Delta Sigmas offer unipolar and bipolar, can have build in PGA
- Can it be adapted externally by OPAs / INAs / resistors?
  - Sometimes external driving circuit is needed anyway
    - SAR and Pipeline: signal can be adapted with this for saving cost and power
  - Consider signal conditioning in combination with single supply converter

# Power consumption

- Power consumption and/or dissipation is generally a concern, but performance needs may demand certain power
- Delta-sigma: allows nice trade-off between resolution, speed and power-consumption
- SARs: are generally the low-power option
- Pipeline ADCs: are relatively power-hungry to achieve their high performance-levels




# Agenda

- Analog-to-Digital-Converters (ADCs)
  - What are the Signal Frequencies
    - Analog Classes of applications
    - Frequency ranges of ADCs
  - Nuts and Bolts of Delta-Sigma Converters
  - The SAR ADC
  - The High-speed Pipeline Topology
- Digital-to-Analog-Converters (DACs)
  - R-2R-DACs
  - String-DACs
  - Multiplying DACs
  - Delta-Sigma DACs
  - High-Speed Current-Steering DACs


# DAC Architectures

- R-2R—The oldest and still the “cleanest” conversion method
- String—A tapped resistor string
- Delta Sigma—(One bit) Trades resolution in amplitude for resolution in time. Requires a system clock that is faster than the bit data

# TI DAC Technologies

 

# Settling time definitions

 


Settling time is influenced by

- accuracy (e.g. 0.003% or 0.1% FS)
- load (capacitive, resistive)
- Digital Code step size

DAC9881 (18b, 5us)	Settling time	To $\pm 0.003\%$ FS, $R_L = 10k\Omega$ , $C_L = 50pF$ , code 1000h to F000h
DAC8564 (16b, 10us)	Output voltage settling time	To $\pm 0.003\%$ FSR, 0200h to FD00h, $R_L = 2k\Omega$ , $0pF < C_L < 200pF$
		$R_L = 2k\Omega$ , $C_L = 500pF$
DAC5681 (16b, 1GSPS)	$t_{s(DAC)}$ Output settling time to 0.1%	Transition: Code 0x0000 to 0xFFFF

# R-2R or Current Segment Topology

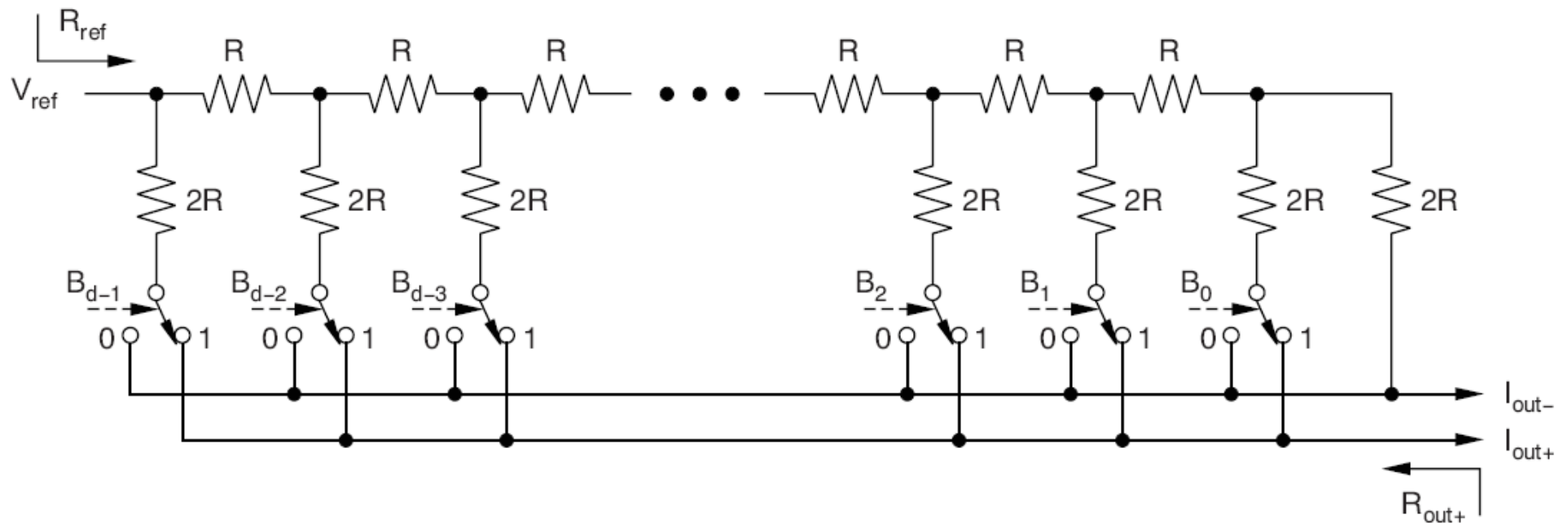

This classical approach delivers a current mode output.  
For voltage mode output, this structure is followed by an I/V converter

# Advantages of R-2R DACs

- Can achieve high performance INL & DNL
- Medium Settling Time Capability
- Low Noise R-2R Ladder

# Disadvantages of R-2R DACs

## Data timing skews


- causing high output glitches
- Need HV transistor input stage for HV DAC Buffer → Low Bandwidth & Settling
- Internally, requires high common mode voltage swing output amp

# Applications for R-2R DACs

- Automatic test equipment
- Precision Instrumentation
- Industrial control
- Data Acquisition systems
- Control Loop systems


 
# Principle Resistor String DAC Architecture



# What is a Resistor String DAC?

- It is basically built with the following:
  - A voltage reference.
  - A set of matched resistors.
  - A set of switches.
  - And an output buffer.
- Control and interface logic, and all other features varies upon design specifications.

# Advantages of String DACs

- Inherently monotonic
- Cost Effective
  - Simple to build (by design)
  - No need for trimming
- Low Glitch Energy
- Good DNL performance

# Disadvantages of String DACs

- Requires  $2^N - 1$  matching resistors
    - Resolution is limited
    - Size can grow with resolution requirement
    - High resolution is achieved by pipeline-like architectures which compromises monotonicity
  - Decoding logic
  - Many interconnections
  - Requires output buffer
  - Accuracy (due to linearity errors)
- } These factors limit the achievable speed of the DAC


# Applications for String DACs

- Control Loops
  - Industrial Control
  - Digital Servos
  - Machine and Motion
- Trimmers
- Instrumentation
- Digital Offset and Gain Adjustment

# String DACs – Not-recommended Applications

- High Speed Applications
- Communications
- Signal Waveform Generation
- Precision Voltage Setting

# Multiplying DAC Architecture

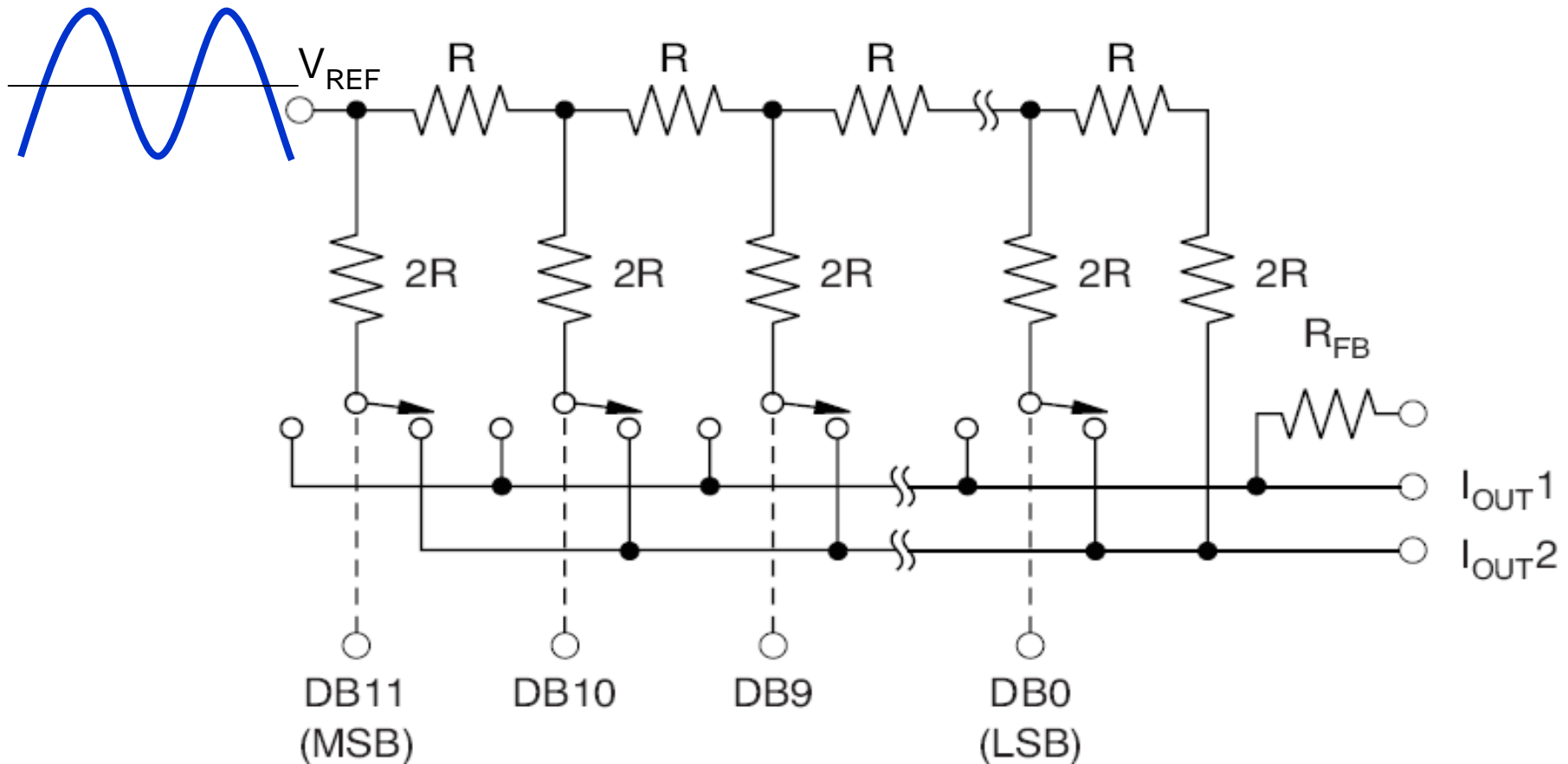

The above structure is essentially a R-2R-architecture. The “invisible” difference is , that  $V_{REF}$  can be an analog signal, i.e. an alternating signal, even crossing zero Volts.


# Multiplying DAC

- Output Amplifier functions
  - Output Amp I/V: Common Mode Voltage @ Fixed 0V
  - High Voltage (HV) capable with external HV-OPA I/V
  - High Bandwidth Capability
- MDAC internal characteristics
  - Can achieve high performance INL & DNL
  - Reference-current is constant
  - Low noise R-2R ladder
  - Flexible reference input (Zero-Crossing, AC-signal)



# MDAC – what is it used for?

- Programmable Attenuation (fixed digital input, reference used as signal-input)

 

DAC8822: attenuation vs. reference multiplying bandwidth at various digital codes


- Selectable Inversion (by inverting the reference)

# Multiplying DAC

## Appropriate applications

- Waveform Generators
- Audio-Applications
- Automatic Test Equipment
- Instrumentation
- Digitally Controlled Calibration
- Industrial Control PLCs

# Delta-Sigma DACs

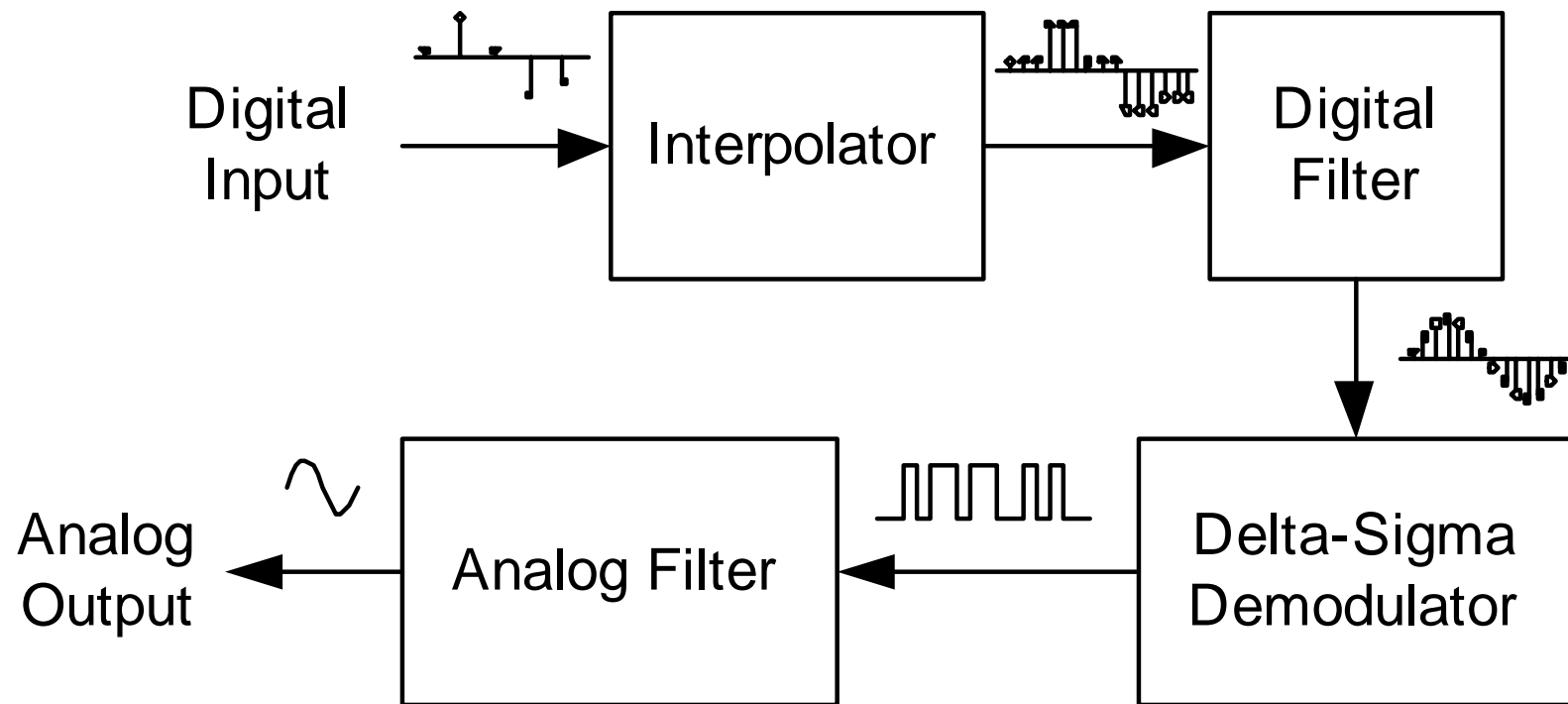

A Delta-Sigma-DAC is basically an DS-ADC operated in reverse direction: Oversampling of the digital input, digital filtering, demodulation, analog filtering. Predominantly used in Audio-DACs.


# Delta-Sigma DAC Properties

- High resolution
  - Low Power
  - Voltage output
  - Good Linearity
  - Low Cost
  - In Audio: moving noise out of audible range
- 
- Settling time ~2ms
  - Long Latency
  - Not optimized for DC

# Delta-Sigma DAC Applications

- Audio-Applications
- Sonar
- Process Control
- ATE Pin Electronics
- Closed-Loop Servo Control
- Smart Transmitters
- Portable Instruments

# Current steering DACs

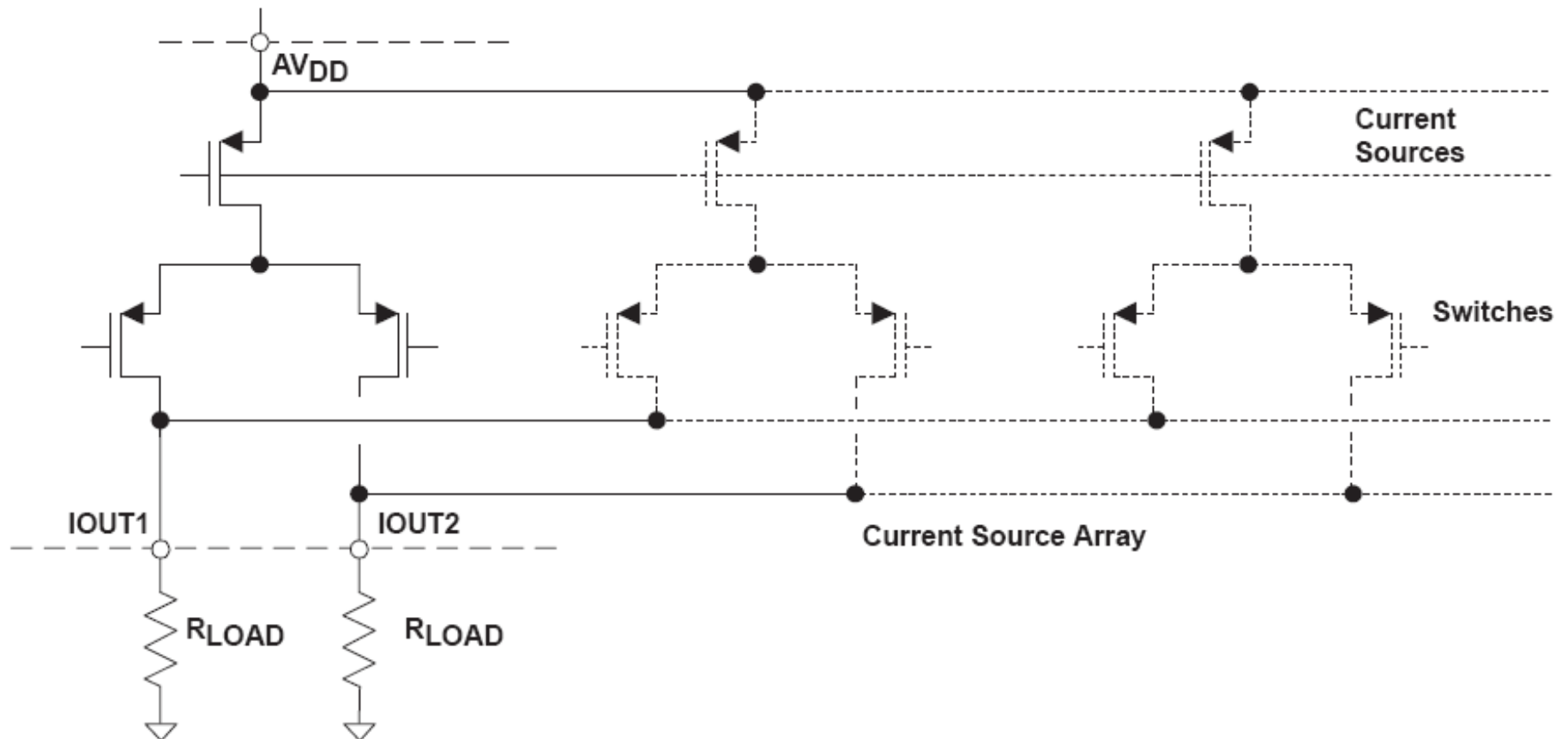

Current steering DACs replace the resistor arrays of R-2R-DACs with weighted current sources

# Current steering DAC

## Properties

- Highest speed (1 GSPS+, 10ns settling time)
  - Best AC-performance
  - 20mA output current (typ)
  - Low complexity, low glitch-energy
- 
- Current output: often I/V-converter or transformer required

# Current steering DAC Applications

- Communication Infrastructure  
(Wireless and Line Communication)
- Test Equipment
- Radar



**Choose the right D/A converter  
for your application**

# Desired resolution and settling time?

- Resolution
  - R2R available up to 18 bits
  - String available up to 16 bit
  - Delta Sigma available up to 24bits (Audio DACS <32bit)
- Settling time
  - Note the differences in definition!
  - What update rates / output frequencies are available?
    - 16 bit -> 1GSPS
    - 18 bit -> for DC-precision
    - 24 bit -> 768kHz (Audio)
    - 32bit -> 192kHz (Audio)
  - Consider over sampling for relaxing the reconstruction filter requirement

# Linearity and Glitches

- Linearity
  - INL, DNL for R2R and String
  - R2R is trimmed, offers very good linearity but high cost
  - String: fair linearity low cost
- Does output glitch energy matter?
  - go for String DACs for lowest glitch
  - some R2R are pretty good but not as good as String DACs

# Integration and Interface

- Multiple outputs
  - 2ch, 4ch, 8ch DACs with synchronous output update
- Reference source?
  - Internal or external fixed Vref
  - External Vref can be variable -> multiplying DACs
- Interface
  - Serial, Parallel, SPI, I2C or High Speed LVDS

# Output voltage range?

- Consider using external Opamps to gain and level shift the output signal – it can save cost in combination with a single supply DAC
- Some DAC have current outputs anyway and a trans-impedance stage is required

# Power consumption

- Power consumption and/or dissipation is determined by the output impedance and drive-strength rather than architecture
- Precision DACs usually have 10kOhm impedance and drive 1mA, i.e. 10mW @ 10V.  
The current is drawn from the reference, hence DACs with internal REF have higher consumption
- Current-Steering DACs for high-speed applications drive 20mA and consequently require higher supply-currents.